```
Problem 14: [6 points] Filename: hw0prob14.sv
```

```
1 `default_nettype none
2 module hw0prob14
3   (input logic a,
4   input logic b,
5   input logic c,
6   output logic p );
7   logic n_b, f1;
8   not g1(n_b, b);
9   and #2 g2(f1, a, n_b);
10   or #3 g3(p, c, f1);
11 endmodule: hw0prob14
```